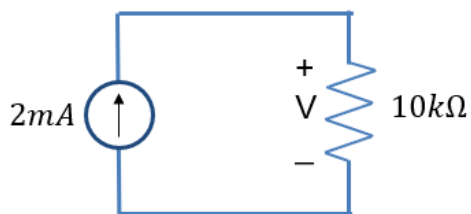



- **Current** is measured **through** an interface
- **Voltage** is measured **between** two points
- **Independent sources** are drawn with a circle. They produce a constant current (arrow) or voltage (plus and minus signs).
- **Resistors** have a linear relationship between its current and voltage, $V = IR$ (known as **Ohm's law**)
- **Kirchhoff's Current Law (KCL)**: The sum of all currents entering (or leaving) any node of a circuit must be zero.
- **Kirchhoff's Voltage Law (KVL)**: The sum of all voltage drops around any closed loop in a circuit must be zero.

 Basic examples

1




2

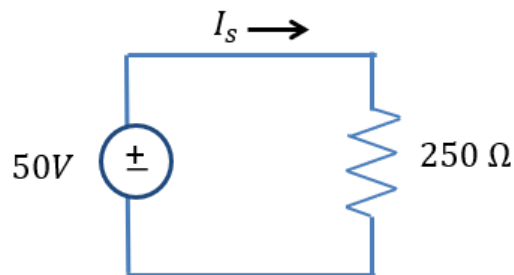


 Try slight variations


3

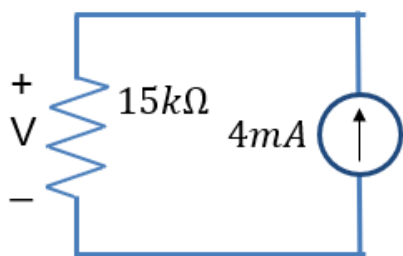


4

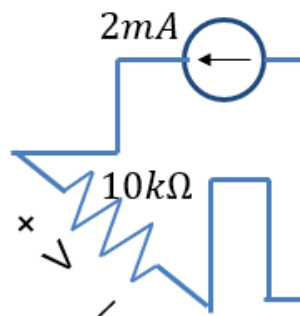


5

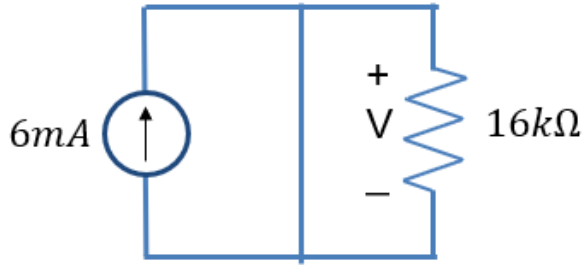


6

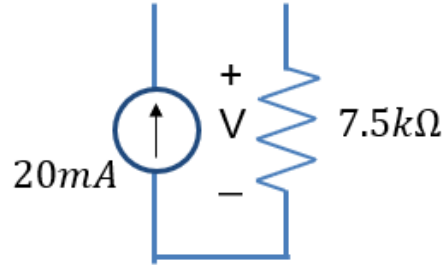


7

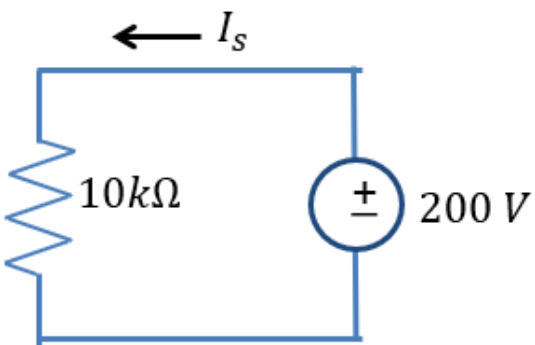


8

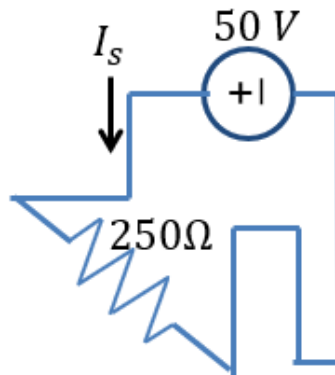

9

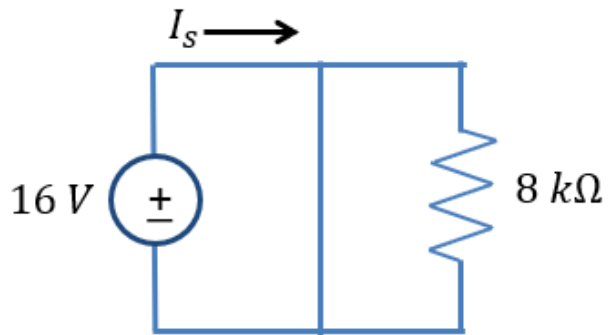


10

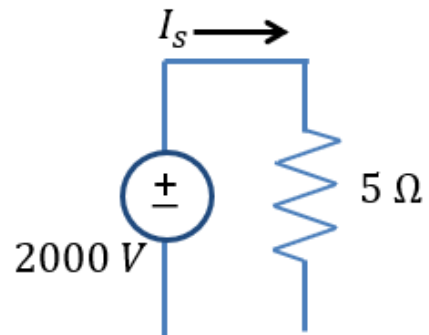


Apply Kirchoff's laws


11

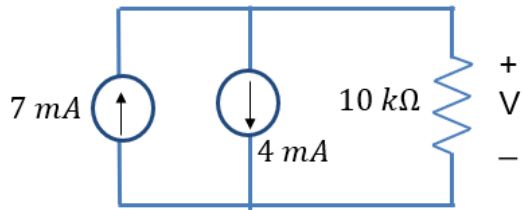


12

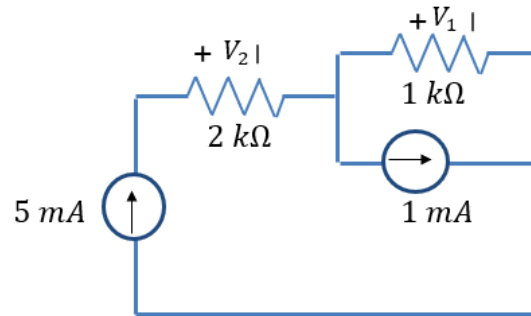

13

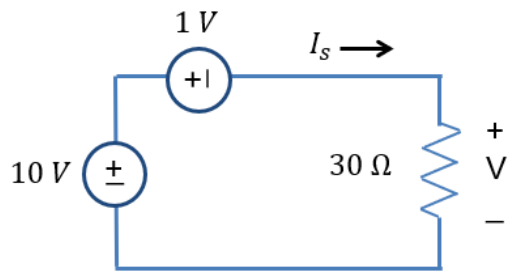


14

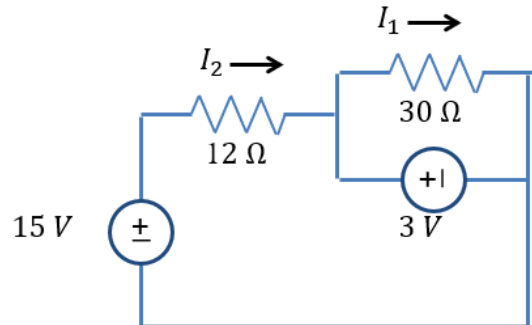


Watch your signs! Ohm's law applies if current is oriented *entering* the resistor where the plus side of the voltage measurement is taken.


15

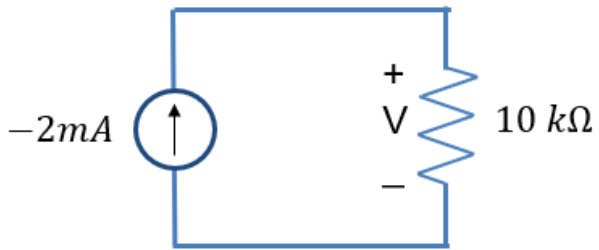


16

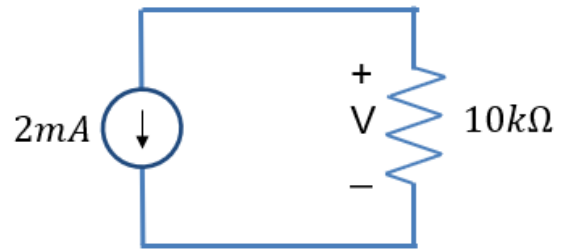

17

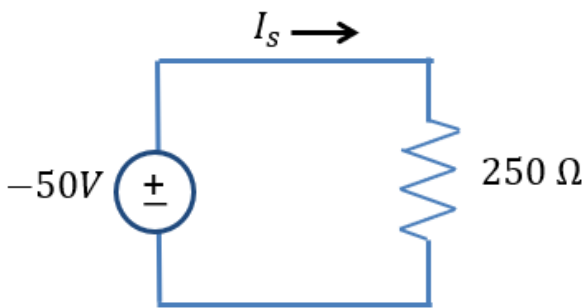

18

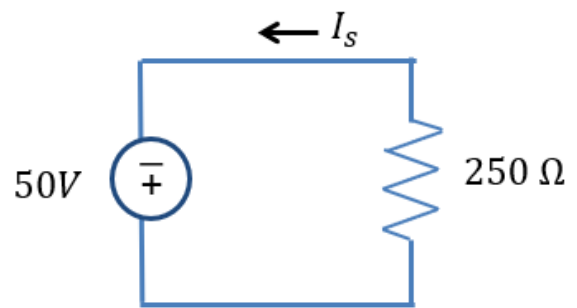

A bigger example

19

