
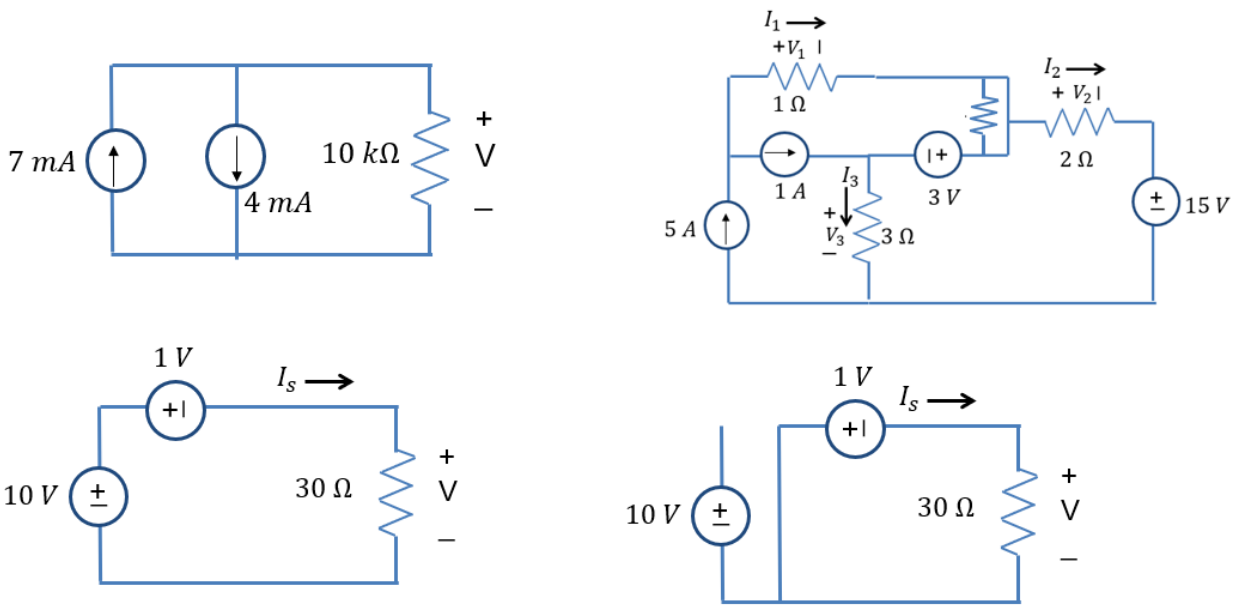


- The **voltage** across a short circuit is **zero**
- The **current** through an open circuit is **zero**
- Elements in **series** share one junction, with nothing else connected to the same junction, and they have the **same current** (KCL)
- Elements in **parallel** share two junctions, regardless of what else is connected, and they have the **same voltage** (KVL)
- Resistors in **series** add
- Resistors in **parallel** combine as:  $R_{\parallel} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$


Find shorts, opens, parallel, series

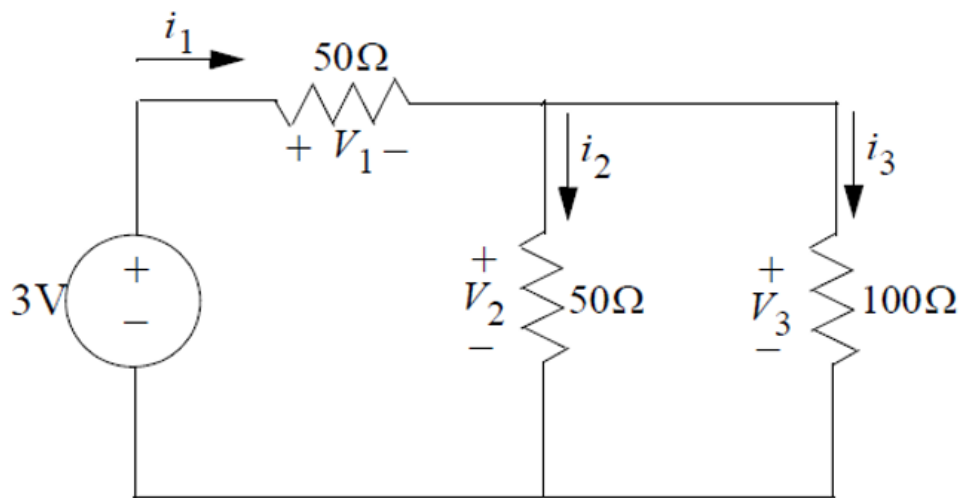


Another KCL example



Dependent source example

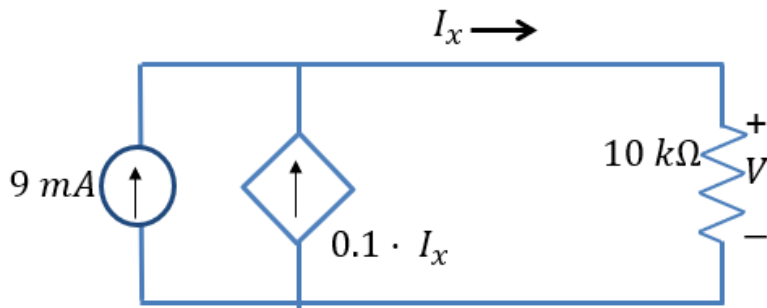

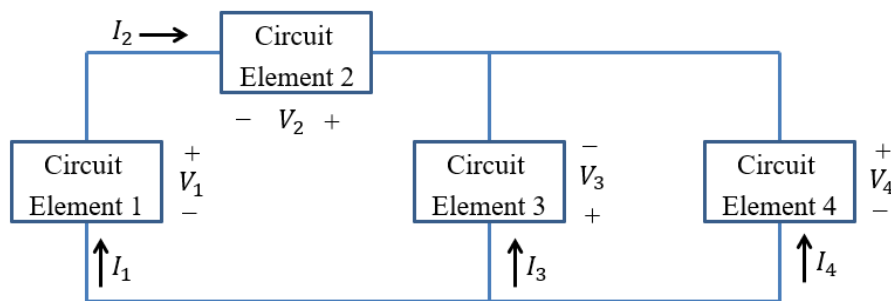Conservation of energy example: what power is consumed by each device?



Element	Voltage	Current
1	3 volts	-1mA
2	-2 volts	-1mA
3	-1 volt	4mA
4	1 volt	-3mA



Element	Power
1	
2	
3	
4	

Source restrictions example: what value of  $V_g$  is necessary for the connection to be valid? With that value, what is the power associated with the 8 A current source?

