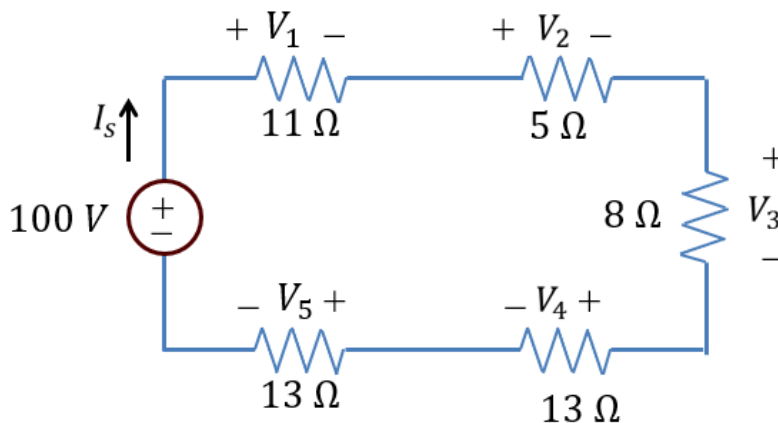


- Series combination: $R_{eq} = R_1 + R_2$
- Parallel combination $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$
- Voltage dividers: $V_1 = V_s \cdot \frac{R_1}{R_1 + R_2}$ and $V_2 = V_s \cdot \frac{R_2}{R_1 + R_2}$
- Current dividers: $V_1 = V_s \cdot \frac{R_2}{R_1 + R_2}$ and $V_2 = V_s \cdot \frac{R_1}{R_1 + R_2}$


Convert delta to wye	Convert wye to delta
$R_1 = \frac{R_b \cdot R_c}{R_a + R_b + R_c}$ $R_2 = \frac{R_a \cdot R_c}{R_a + R_b + R_c}$ $R_3 = \frac{R_a \cdot R_b}{R_a + R_b + R_c}$	$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$ $R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$ $R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$

- Measure voltage across device or between two nodes
- Measure current by breaking circuit
- Measure resistance with Wheatstone bridge


Solve for I_s and the voltage across each resistor



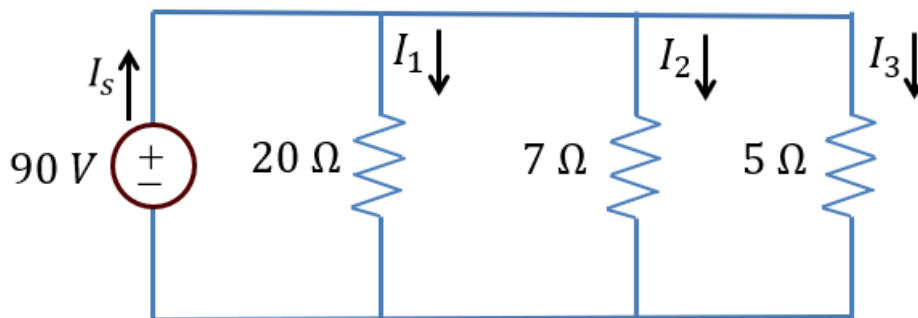
Solve for I_s and the current through each resistor



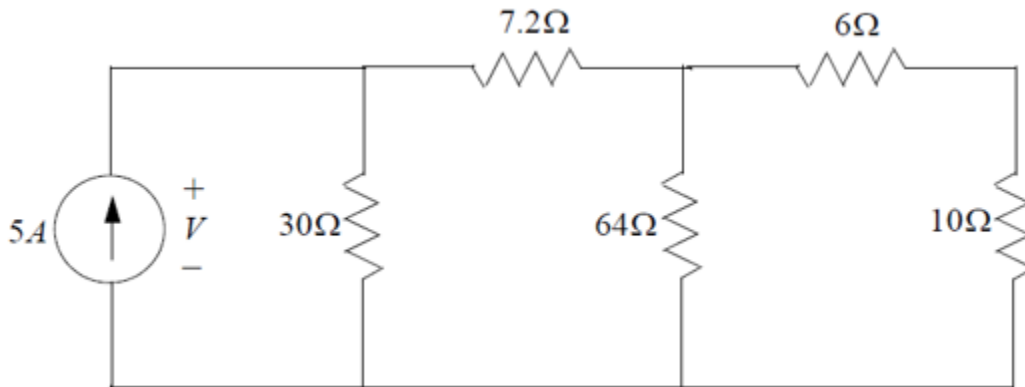Find the voltage V , the power delivered by the source, and power dissipated in the 10Ω resistor



Examples of voltage and current dividers

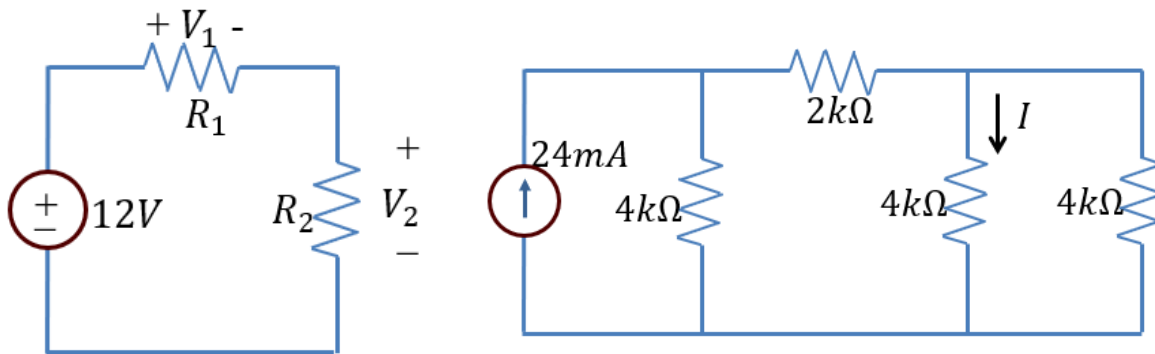

Example of delta-wye transformation

