

Class 17: Phasor analysis for AC circuits


The effect of resistors, inductors, and capacitors upon phasors is handled with a concept known as **impedance**. Impedance (Z) basically acts like a complex resistance. $V = I \cdot Z$

The impedance of inductors and capacitors depends on frequency


$\omega = 2\pi f$. Almost all of the resistive circuit analysis methods you learned for DC apply.

Element	Time Domain	Phasor Domain	Z (impedance)
Resistor	$v(t) = Ri(t)$	$\mathbf{V} = \mathbf{I}R$	R
Inductor	$v(t) = L \frac{di(t)}{dt}$	$\mathbf{V} = j\omega L \mathbf{I}$	$j\omega L$
Capacitor	$i(t) = C \frac{dv(t)}{dt}$	$\mathbf{V} = \frac{1}{j\omega C} \mathbf{I}$	$\frac{1}{j\omega C}$


Example 1: Find the current phasor \mathbf{I} for this 1 kHz circuit

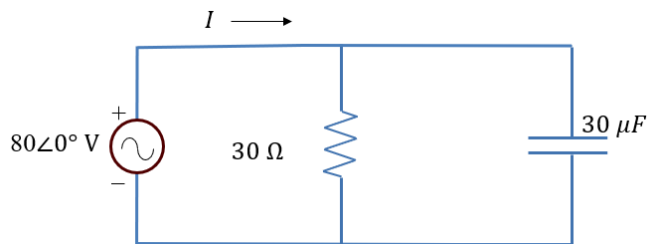

Example 2: Solve for the phasor V_c for this circuit if it is operated at 400 Hz

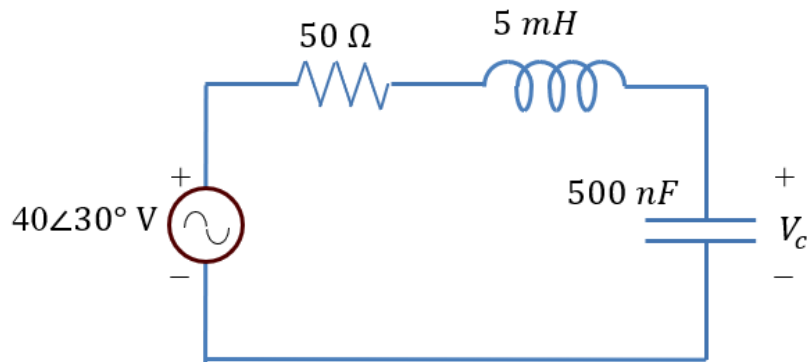

Example 3: Solve for the phasor I_1 . The impedance for Z_c is given so you don't need the frequency.

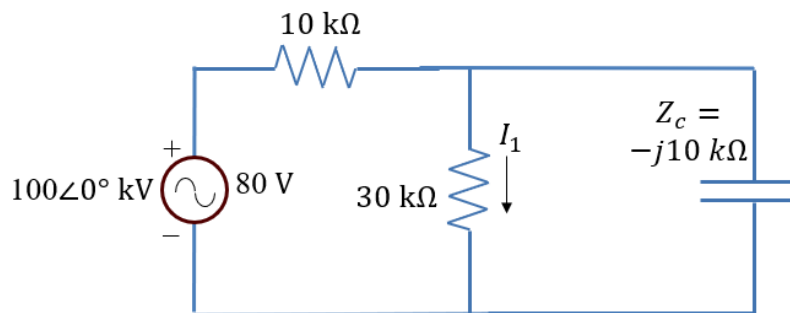

Example 4:

$$i_s(t) = 7.1 \cos(1256t - 10^\circ) \text{ A}$$
$$v_s(t) = 113.1 \cos(1256t + 45^\circ) \text{ V}$$

Find the time signal $v_1(t)$. (Try using mesh-current analysis and node-voltage analysis.)

