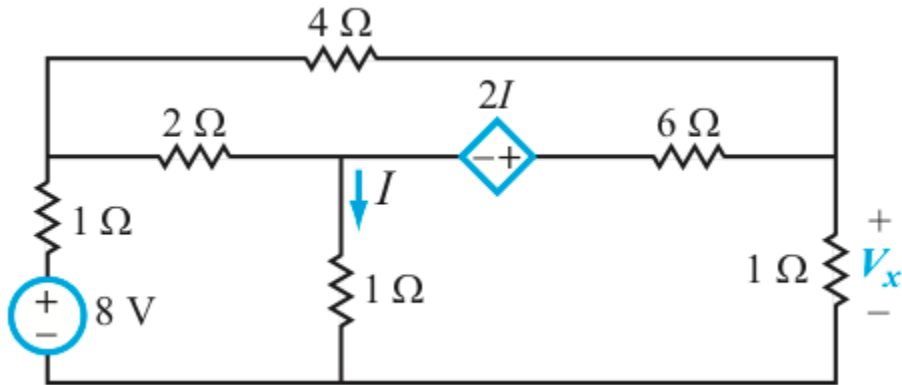
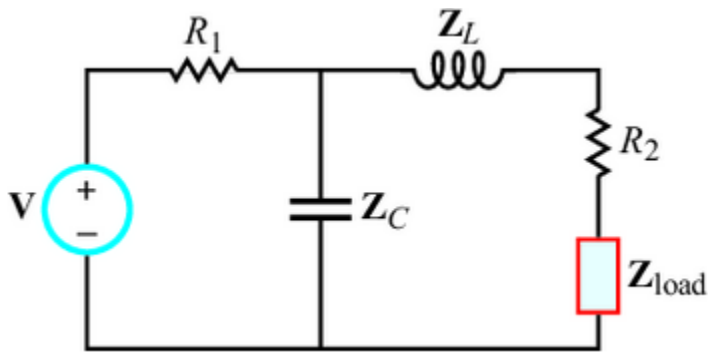


DC with dependent source: determine  $V_x$  in the circuit below.



AC Thevenin equivalent and maximum power transfer: choose the load impedance such that the power dissipated in it is maximized. How much power will that be?

$$V = 20\angle 0^\circ \text{V}; R_1 = 10\Omega, R_2 = 5\Omega, Z_C = -j5\Omega; Z_L = j3\Omega$$



Second order transient. Determine  $v_C(t)$  for  $t > 0$ .

