- A phasor is a complex number that represents a cosine-valued AC function
- The Root Mean Square (RMS) for cosine is found by dividing the maximum value by $\sqrt{2}$
- In polar form, $R \ge \theta$, a phasor represents the RMS voltage or current and phase angle - $R \ge \theta \rightarrow \sqrt{2} R \cos(2\pi f t + \theta)$
- Conversions to rectangular form: a+jb, and back can be done with these identities:

$$R = \sqrt{a^2 + b^2}$$
 $\theta = aTan\left(\frac{b}{a}\right)$ $a = R\cos\theta$ $b = R\sin\theta$

- Complex number addition can be done in rectangular form, and complex number multiplication can be done in polar form.
- Phasor diagrams have the real part on the x axis and imaginary part on the y axis.
- The angular frequency is $\omega = 2\pi f$.
- KVL, KCL, and Ohm's law all apply with AC phasor analysis exactly as with DC.
- The effect of resistors, inductors, and capacitors upon phasors is handled with impedance (Z), which acts like complex resistance. V = I · Z
- The impedance of inductors and capacitors depends on frequency
- Instantaneous power from the time signal p(t) = v(t)i(t)
- Complex power: $S = VI^* = |S| \ge \theta_s = P + jQ$ Don't forget the conjugate!! (*)
- Average power or active power or real power: $\operatorname{Re}[S] = P = |S| \cos \theta_s$
 - This is what's normally thought of as "power". Units are W.
 - It's also what you get if you take the average value of the instantaneous power
- Reactive power: $\text{Im}[S] = Q = |S| \sin \theta_s$
- Apparent power: $|S| = |V| \cdot |I|$
- Power factor angle: θ_s is the angle of *S* or $\theta_v \theta_i$
- **Power factor**: $\cos(\theta_s) = P/|S|$. It must be indicated as "leading" (negative θ_s) or "lagging" (positive θ_s). A unity (1) power factor indicates zero reactive power and is neither leading nor lagging.
- At every node in the system, both active (real) and reactive power are conserved
- Inductors only absorb reactive power, capacitors only produce reactive power
- Capacitor banks are used for power factor correction by supplying reactive power locally
- A three-phase system is **balanced** if (1) all voltages are equal in magnitude and shifted in phase by 120°, (2) loads are equal on each phase, (3) impedances are equal on each phase.
- Line-to-line voltages are related to line-to-neutral (phase) voltages as: $V_{phase} = \frac{V_{line}}{\sqrt{3} \angle 30^{\circ}}$
- Delta-connected loads can be replaced with wye-connected loads: $Z_Y = \frac{1}{3}Z_{\Delta}$
- Delta-connected sources can be replaced by wye-connected sources $V_{phase} = \frac{V_{line}}{\sqrt{3} \angle 30^{\circ}}$
- Per-phase analysis works for balanced systems if there is no mutual inductance between phases. Steps: (1) convert delta sources and loads to equivalent wye (2) solve phase "a" circuit independent of other phases (3) total system power is $3V_aI_a^*$ (4) if needed, go back to original circuit to find "b" or "c" values and internal Δ values.

Element	Time Domain	Phasor Domain	Z (impedance)
Resistor	v(t) = Ri(t)	V = IR	R
Inductor	$v(t) = L \frac{di(t)}{dt}$	$\boldsymbol{V} = j\omega L \boldsymbol{I}$	jωL
Capacitor	$i(t) = C \frac{dv(t)}{dt}$	$\boldsymbol{V} = \frac{1}{j\omega C}\boldsymbol{I}$	$\frac{1}{j\omega C}$

Units are "var".

Units are "VA".

Homework #1 due Tuesday, Jan 24th Solutions

1. Practice problems for phasor conversion (solutions not given)

2. Solve for *I* as a phasor using any method. Assuming the frequency is 60 Hz, write the time signals for *V* and *I*.

- Solve for I as a phasor using any method
- Assuming the frequency is 1 kHz, write the time signals for V and I

Fy = VS 12.2KA

 $V_{Y} = 4k \cdot T_{Y} = V_{s} \frac{Y}{12.2}$ $T = \frac{V_{s}}{R} = V_{s} \frac{4}{12.2 \cdot 14k}$

I = 0.324 < 40' A

 $13.2 \angle 110^{\circ} kV \longrightarrow 6k\Omega \longrightarrow 14k\Omega I \longrightarrow 14$

 $8k\Omega$

 $v(t) = 13.2\sqrt{2}\cos(2\pi 60t + 110^\circ) \text{ kV}$ $i(t) = 0.324\sqrt{2}\cos(2\pi 60t + 110^\circ) \text{ kV}$

3.

ź

- Find the current phasor I for this 1 kHz circuit
- Impedance of the resistor? $Z = 30 \Omega$
- Impedance of the capacitor?

$$Z = \frac{1}{j\omega C} = \frac{1}{j2\pi 1k \cdot 30\mu} = -j5.3\Omega$$

• You can treat impedances just like complex resistances! The capacitor and resistor are in parallel

$$Z = \frac{1}{\frac{1}{30} + \frac{1}{-j5.3}} = (0.91 - j5.14) \Omega$$
$$I = \frac{V}{Z} = \frac{80}{0.91 - j5.14} = 15.32 \angle 80^{\circ} A$$



What would this be as a time function? What would it be in a lower frequency?

4.

Solve for the phasor V_c for this circuit if it is operated at 400 Hz



• •

5. (Solution not given.)



7. (Solution not given – quite similar to online video.)

8.

