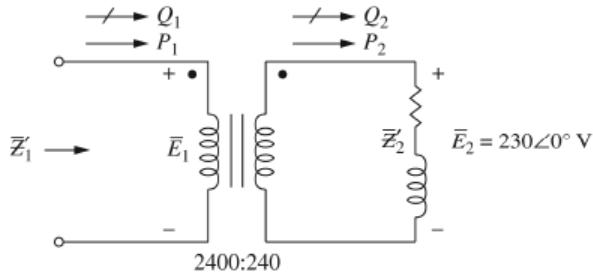


Homework 3 Solutions

3.4



$$(a) \quad E_1 = \frac{N_1}{N_2} E_2 = \frac{2400}{240} (230) = 2300 \text{ V}$$

$$(b) \quad \bar{S}_2 = \bar{E}_2 \bar{I}_2^*; \bar{I}_2 = \left(\frac{\bar{S}_2}{\bar{E}_2} \right)^* = \left[\frac{60 \times 10^3 \angle \cos^{-1} 0.8}{230 \angle 0^\circ} \right]^* = 260.9 \angle -36.87^\circ$$

$$\begin{aligned} \bar{Z}_2 &= \frac{\bar{E}_2}{\bar{I}_2} = \frac{230 \angle 0^\circ}{260.9 \angle -36.87^\circ} = 0.8817 \angle 36.87^\circ \Omega \\ &= 0.705 + j.529 \Omega \end{aligned}$$

$$(c) \quad \bar{Z}'_1 = \left(\frac{N_1}{N_2} \right)^2 \bar{Z}_2 = 100 \bar{Z}_2 = 88.17 \angle 36.87^\circ \Omega$$

$$(d) \quad P_1 = P_2 = 60(0.8) = 48 \text{ kW}$$

$$Q_1 = Q_2 = 48 \tan(36.87^\circ) = 36 \text{ kVAR}$$

- 3.23 Select a common base of 100MVA and 22kV on the generator side; Base voltage at bus 1 is 22kV; this fixes the voltage bases for the remaining buses in accordance with the transformer turns ratios. Using Eq. 3.3.11, per-unit reactances on the selected base are given by

$$G : X = 0.18 \left(\frac{100}{90} \right) = 0.2; T_1 : X = 0.1 \left(\frac{100}{50} \right) = 0.2$$

$$T_2 : X = 0.06 \left(\frac{100}{40} \right) = 0.15; T_2 : X = 0.06 \left(\frac{100}{40} \right) = 0.15$$

$$T_3 : X = 0.064 \left(\frac{100}{40} \right) = 0.16; T_4 : X = 0.08 \left(\frac{100}{40} \right) = 0.2$$

$$M : X = 0.185 \left(\frac{100}{66.5} \right) \left(\frac{10.45}{11} \right)^2 = 0.25$$

$$\text{For Line 1, } Z_{\text{BASE}} = \frac{(220)^2}{100} = 484 \Omega \text{ and } X = \frac{48.4}{484} = 0.1$$

$$\text{For Line 2, } Z_{\text{BASE}} = \frac{(110)^2}{100} = 121 \Omega \text{ and } X = \frac{65.43}{121} = 0.54$$

The load complex power at 0.6 Lagging pf is $\bar{S}_{L(3\phi)} = 57 \angle -53.13^\circ \text{ MVA}$

$$\begin{aligned} \therefore \text{The load impedance in OHMS is } \bar{Z}_L &= \frac{(10.45)^2}{57 \angle -53.13^\circ} = \frac{V_L^2}{\bar{S}_{L(3\phi)}^*} \\ &= 1.1495 + j1.53267 \Omega \end{aligned}$$

The base impedance for the load is $(11)^2 / 100 = 1.21 \Omega$

$$\therefore \text{Load Impedance in pu} = \frac{1.1495 + j1.53267}{1.21} = 0.95 + j1.2667$$

The per-unit equivalent circuit is shown below:

