

Homework #1 due Tuesday, Jan 23rd

For more help, read Chapters 1 and 2 in the textbook, view the videos and slides on the website, and take advantage of office hours of TAs and the instructor.

1. Solutions not given.

2. Solve for I as a phasor using any method. Assuming the frequency is 60 Hz, write the time signals for V and I .


- Solve for I as a phasor using any method
- Assuming the frequency is 1 kHz, write the time signals for V and I

$$I_4 = \frac{V_s}{12.2k\Omega}$$

$$V_4 = 4k \cdot I_4 = V_s \frac{4}{12.2}$$

$$I = \frac{V}{R} = V_s \frac{4}{12.2 \cdot 14k}$$

$$I = 0.324 \angle 110^\circ \text{ A}$$

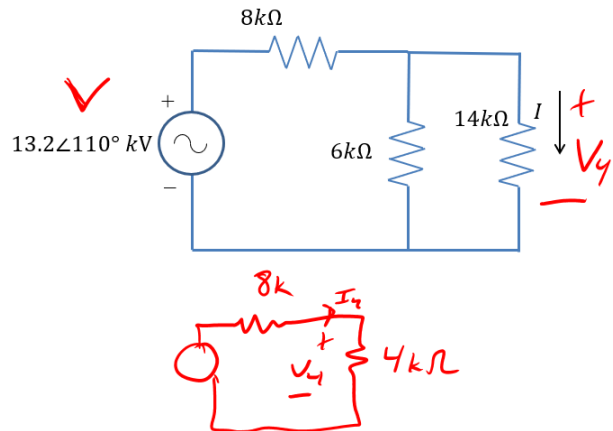

$$v(t) = 13.2\sqrt{2} \cos(2\pi 60t + 110^\circ) \text{ kV}$$


$$i(t) = 0.324\sqrt{2} \cos(2\pi 60t + 110^\circ) \text{ kV}$$

3.

- Find the current phasor I for this 1 kHz circuit
- Impedance of the resistor?
 $Z = 30 \Omega$
- Impedance of the capacitor?
 $Z = \frac{1}{j\omega C} = \frac{1}{j2\pi 1k \cdot 30\mu} = -j5.3\Omega$
- You can treat impedances just like complex resistances! The capacitor and resistor are in parallel

$$Z = \frac{1}{\frac{1}{30} + \frac{1}{-j5.3}} = (0.91 - j5.14) \Omega$$
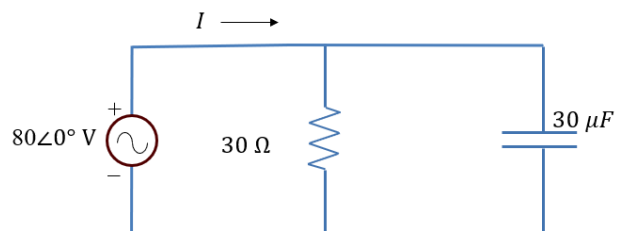
$$I = \frac{V}{Z} = \frac{80}{0.91 - j5.14} = 15.32 \angle 80^\circ \text{ A}$$



What would this be as a time function?
What would it be in a lower frequency?

4. Solve for the phasor V_C for this circuit if it is operated at 400 Hz

Handwritten calculations:

$$Z_R = 50 \Omega$$

$$Z_L = j12.566 \Omega$$

$$Z_C = -j715.77 \Omega$$

$$Z = 50 - j783.2 \Omega$$



$$I = \frac{V}{Z} = \frac{40 \angle 30^\circ \text{ V}}{50 - j783.2} = .051 \angle 116^\circ \text{ A}$$

$$V_C = I \cdot Z_C = (.051 \angle 116^\circ)(-j715) = 40 \angle 30^\circ \text{ V} \cdot 784 \angle -86^\circ = 40 \angle 26^\circ \text{ V}$$

5. Solution not given.

6. Calculate for the voltage source

1. Current I
2. Complex power $S = VI^* = 698 \angle 14^\circ \text{ VA} = 677 + j169$
3. Active power $P = (120 \angle 30^\circ)(5.92 \angle 16^\circ)^* = 677 \text{ W}$
4. Reactive power $Q = 168.9 \text{ var}$
5. Apparent power $|S| = 698 \text{ VA}$
6. Power factor angle $\theta_s = 14^\circ$
7. Power factor 0.97 lagging

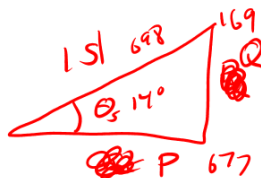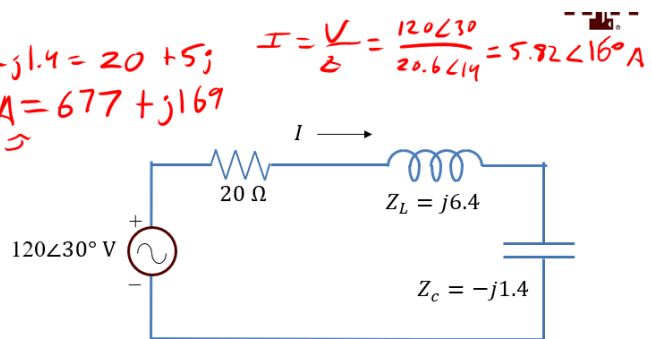



Bonus: Can you verify conservation of both active and reactive power?

7. Solutions not given – quite similar to online video.

8.

We want to find

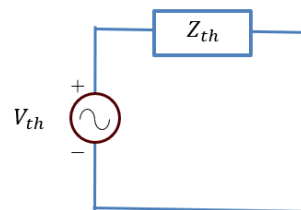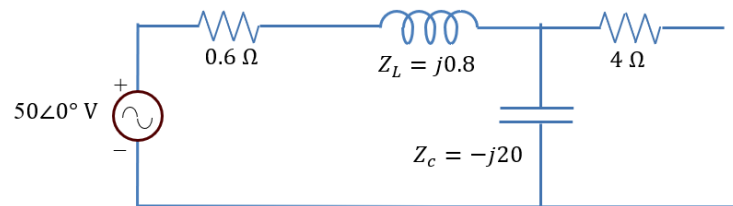- (1) The Thevenin equivalent for this circuit, as shown.
- (2) The maximum power that could be delivered to a load with impedance Z_{load}



Maximum power transfer occurs when $Z_{load} = Z_{th}^*$

$$\begin{aligned}
 V_{th} &= 52.06 \angle -1.79^\circ \text{ V} \\
 Z_{th} &= 4.65 + j0.81 \ \Omega \\
 S_{Max} &= 145.69 - j25.47 \text{ W}
 \end{aligned}$$

Homework #2 due Tuesday, Jan 30th

Textbook problems:

2.9

$$\begin{aligned}
 KVL: 120 \angle 0^\circ &= (60 \angle 0^\circ)(0.1 + j0.5) + \bar{V}_{LOAD} \\
 \therefore \bar{V}_{LOAD} &= 120 \angle 0^\circ - (60 \angle 0^\circ)(0.1 + j0.5) \\
 &= 114.1 - j30.0 = 117.9 \angle -14.7^\circ \text{ V}
 \end{aligned}$$

2.22

$$(a) \bar{Y}_1 = \frac{1}{\bar{Z}_1} = \frac{1}{(4 + j5)} = \frac{1}{6.4 \angle 51.34^\circ} = 0.16 \angle -51.34^\circ \\ = (0.1 - j0.12) \text{ S}$$

$$\bar{Y}_2 = \frac{1}{\bar{Z}_2} = \frac{1}{10} = 0.1 \text{ S}$$

$$P = V^2(G_1 + G_2) \Rightarrow V = \sqrt{\frac{P}{G_1 + G_2}} = \sqrt{\frac{1000}{(0.1 + 0.1)}} = 70.71 \text{ V}$$

$$P_1 = V^2 G_1 = (70.71)^2 0.1 = 500 \text{ W}$$

$$P_2 = V^2 G_2 = (70.71)^2 0.1 = 500 \text{ W}$$

$$(b) \bar{Y}_{eq} = \bar{Y}_1 + \bar{Y}_2 = (0.1 - j0.12) + 0.1 = 0.2 - j0.12 \\ = 0.233 \angle -30.96^\circ \text{ S}$$

$$I_S = V Y_{eq} = 70.71(0.233) = 16.48 \text{ A}$$

2.28

$$\bar{S}_1 = 15 + j6.667$$

$$\bar{S}_2 = 3(0.96) - j3[\sin(\cos^{-1} 0.96)] = 2.88 - j0.84$$

$$\bar{S}_3 = 15 + j0$$

$$\bar{S}_{TOTAL} = \bar{S}_1 + \bar{S}_2 + \bar{S}_3 = (32.88 + j5.827) \text{ kVA}$$

(i) Let \bar{Z} be the impedance of a series combination of R and X

$$\text{Since } \bar{S} = \bar{V} \bar{I}^* = \bar{V} \left(\frac{\bar{V}}{\bar{Z}} \right)^* = \frac{V^2}{\bar{Z}^*}, \text{ it follows that}$$

$$\bar{Z}^* = \frac{V^2}{\bar{S}} = \frac{(240)^2}{(32.88 + j5.827)10^3} = (1.698 - j0.301) \Omega \\ \therefore \bar{Z} = (1.698 + j0.301) \Omega \leftarrow$$

(ii) Let \bar{Z} be the impedance of a parallel combination of R and X

$$\text{Then } R = \frac{(240)^2}{(32.88)10^3} = 1.7518 \Omega$$

$$X = \frac{(240)^2}{(5.827)10^3} = 9.885 \Omega$$

$$\therefore \bar{Z} = (1.7518 \parallel j9.885) \Omega \leftarrow$$


Class 1: Three-Phase AC Power Calculations – Selected Solutions

2.43

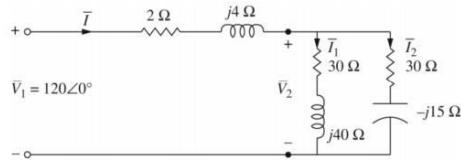- (a) Transforming the Δ -connected load into an equivalent Y , the impedance per phase of the equivalent Y is

$$\bar{Z}_2 = \frac{60 - j45}{3} = (20 - j15) \Omega$$

With the phase voltage $V_1 = \frac{120\sqrt{3}}{\sqrt{3}} = 120 \text{ V}$ taken as a reference, the per-phase equivalent circuit is shown below:



Total impedance viewed from the input terminals is

$$\bar{Z} = 2 + j4 + \frac{(30 + j40)(20 - j15)}{(30 + j40) + (20 - j15)} = 2 + j4 + 22 - j4 = 24 \Omega$$

$$\bar{I} = \frac{\bar{V}_1}{\bar{Z}} = \frac{120 \angle 0^\circ}{24} = 5 \angle 0^\circ \text{ A}$$

The three-phase complex power supplied = $\bar{S} = 3\bar{V}_1 \bar{I}^* = 1800 \text{ W}$

$P = 1800 \text{ W}$ and $Q = 0 \text{ VAR}$ delivered by the sending-end source

- (d) The three-phase complex power absorbed by each load is

$$\bar{S}_1 = 3\bar{V}_2 \bar{I}_1^* = 430 \text{ W} + j600 \text{ VAR}$$

$$\bar{S}_2 = 3\bar{V}_2 \bar{I}_2^* = 1200 \text{ W} - j900 \text{ VAR}$$

The three-phase complex power absorbed by the line is

$$\bar{S}_L = 3(R_L + jX_L)I^2 = 3(2 + j4)(5)^2 = 150 \text{ W} + j300 \text{ VAR}$$


The sum of load powers and line losses is equal to the power delivered from the supply:

$$\begin{aligned} \bar{S}_1 + \bar{S}_2 + \bar{S}_L &= (430 + j600) + (1200 - j900) + (150 + j300) \\ &= 1800 \text{ W} + j0 \text{ VAR} \end{aligned}$$

Class 1: Three-Phase AC Power Calculations – Selected Solutions

2.48

(a)

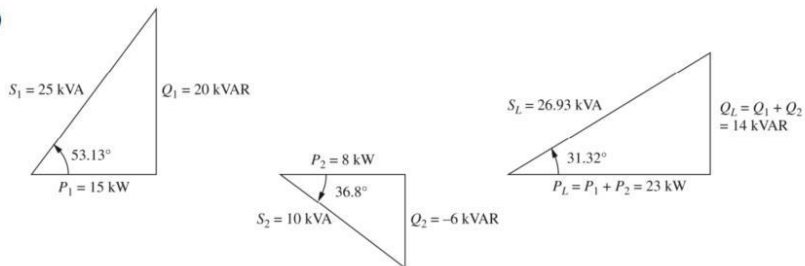(b) $pf = \cos 31.32^\circ = 0.854$ Lagging

$$(c) I_L = \frac{S_L}{\sqrt{3}V_{LL}} = \frac{26.93 \times 10^3}{\sqrt{3}(480)} = 32.39 \text{ A}$$

$$(d) Q_C = Q_L = 14 \times 10^3 \text{ VAR} = 3(V_{LL})^2 / X_\Delta$$

$$X_\Delta = \frac{3(480)^2}{14 \times 10^3} = 49.37 \Omega$$

$$(e) I_C = V_{LL} / X_\Delta = 480 / 49.37 = 9.72 \text{ A}$$

$$I_{LINE} = \frac{P_L}{\sqrt{3} V_{LL}} = \frac{23 \times 10^3}{\sqrt{3} 480} = 27.66 \text{ A}$$

6. Solutions not given.