

ECEN 460, Spring 2026

Power System Operation and Control

Class 6: Transformers, Part 2

Prof. Adam Birchfield

Dept. of Electrical and Computer Engineering

Texas A&M University

abirchfield@tamu.edu



TEXAS A&M
UNIVERSITY

Homework 3 and 4




- No homework on generators. Make sure you understand the lecture notes and labs 2 and 3 (starting this week).
- Homework 3 on transformers: book problems 3.4, 3.5, 3.23, due Feb. 3rd.
- Homework 4 on transmission lines: book regular problems 4.10, 4.11, 4.20, and 4.41, 5.14 (a,b), 5.38, and 5.41 (a,b), due Feb. 10th.

Non-Ideal Transformer Example



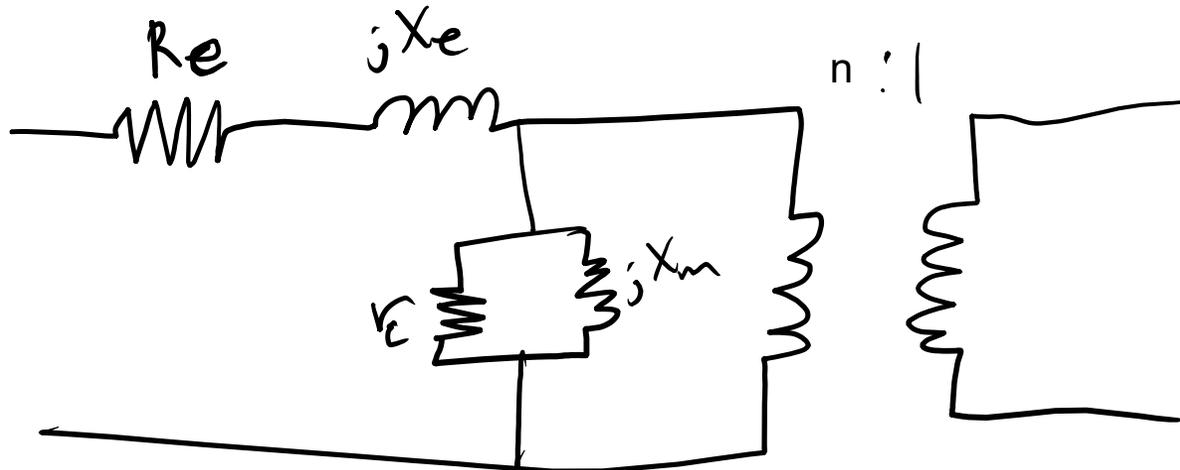- Example: A single phase, 15 MVA, 35/13 kV transformer has the following test data:
 - open circuit: 14 amps, with 3 kW losses
 - short circuit: 6 kV, with 200 kW losses
- Determine the model parameters.



Transformer Example, Cont'd



From the short circuit test

$$I_{sc} = \frac{15 MVA}{35 kV} = 429 \text{ A}, |R_e + jX_e| = \frac{6 \text{ kV}}{429 \text{ A}} = 14 \Omega$$

$$P_{sc} = R_e I_{sc}^2 = 500 \text{ kW} \rightarrow R_e = 1.09 \Omega,$$

$$\text{Hence } X_e = \sqrt{14^2 - 1^2} = 14 \Omega$$

From the open circuit test

$$R_c = \frac{35 \text{ kV}^2}{3 \text{ kW}} = 0.408 \text{ M}\Omega$$

$$|R_e + jX_e + jX_m| = \frac{35 \text{ kV}}{14 \text{ A}} = 2500 \Omega \quad X_m = 2500 \Omega$$

Per Unit Change of MVA Base



- Parameters for equipment are often given using power rating of equipment as the MVA base
- To analyze a system all per unit data must be on a common power base

$$Z_{pu}^{OriginalBase} \rightarrow Z_{actual} \rightarrow Z_{pu}^{NewBase}$$

$$\text{Hence } Z_{pu}^{OriginalBase} \times \frac{V_{base}^2}{S_{Base}^{OriginalBase}} / \frac{V_{base}^2}{S_{Base}^{NewBase}} = Z_{pu}^{NewBase}$$

$$Z_{pu}^{OriginalBase} \times \frac{S_{Base}^{NewBase}}{S_{Base}^{OriginalBase}} = Z_{pu}^{NewBase}$$

Per Unit Change of Base Example



- A 54 MVA transformer has a leakage reactance of 3.69%. What is the reactance on a 100 MVA base?

$$X_e = 0.0369 \times \frac{100}{54} = 0.0683 \text{ p.u.}$$

Transformer Reactance



- Transformer reactance is often specified as a percentage, say 10%. This is a per unit value (divide by 100) on the power base of the transformer.
- Example: A 350 MVA, 230/20 kV transformer has leakage reactance of 10%. What is p.u. value on 100 MVA base? What is value in ohms (230 kV)?

$$X_e = 0.10 \times \frac{100}{350} = 0.0286 \text{ p.u.}$$

$$0.0286 \times \frac{230^2}{100} = 15.1 \text{ } \Omega$$

Three Phase Per-Unit



- Procedure is very similar to 1 phase except we use a 3 phase VA base, and use line to line voltage bases
- Pick a 3ϕ VA base for the entire system $S_B^{3\phi}$
- Pick a voltage base for each different voltage level, V_B . Voltages are line to line.
- Calculate the impedance base

$$Z_B = \frac{V_{B,LL}^2}{S_B^{3\phi}} = \frac{(\sqrt{3} V_{B,LN})^2}{3S_B^{1\phi}} = \frac{V_{B,LN}^2}{S_B^{1\phi}}$$

Exactly the same impedance bases as with single phase!

Three Phase Per-Unit, Cont'd



- Calculate the current base, I_B

$$I_B^{3\phi} = \frac{S_B^{3\phi}}{\sqrt{3} V_{B,LL}} = \frac{3 S_B^{1\phi}}{\sqrt{3} \sqrt{3} V_{B,LN}} = \frac{S_B^{1\phi}}{V_{B,LN}} = I_B^{1\phi}$$

Exactly the same current bases as with single phase!

But, be careful in using 3ph bases to calculate it (need a root 3)

- Convert actual values to per unit

Three Phase Per-Unit Example



- Solve for the current, load voltage and load power in the previous circuit, assuming a 3ϕ power base of 300 MVA, and line to line voltage bases of 13.8 kV, 138 kV and 27.6 kV (square root of 3 larger than the 1 ϕ example voltages). Also assume the generator is Y-connected so its line to line voltage is 13.8 kV.



Convert to per unit as before. Note the system is exactly the same!

3 ϕ Per-Unit Example, Cont'd



- $I = \frac{1.0\angle 0^\circ}{3.91 + j2.327} = 0.22\angle -30.8^\circ$ p.u. (not amps)
 $V_L = 1.0\angle 0^\circ - 0.22\angle -30.8^\circ \times 2.327\angle 90^\circ$
 $= 0.859\angle -30.8^\circ$ p.u.
 $S_L = V_L I_L^* = \frac{|V_L|^2}{Z} = 0.189$ p.u.
 $S_G = 1.0\angle 0^\circ \times 0.22\angle 30.8^\circ = 0.22\angle 30.8^\circ$ p.u.

Again, analysis is exactly the same!

3 ϕ Per-Unit Example, Cont'd 2



Differences appear when we convert back to actual values

$$V_L^{\text{Actual}} = 0.859 \angle -30.8^\circ \times 27.6 \text{ kV} = 23.8 \angle -30.8^\circ \text{ kV}$$

$$S_L^{\text{Actual}} = 0.189 \angle 0^\circ \times 300 \text{ MVA} = 56.7 \angle 0^\circ \text{ MVA}$$

$$S_G^{\text{Actual}} = 0.22 \angle 30.8^\circ \times 300 \text{ MVA} = 66.0 \angle 30.8^\circ \text{ MVA}$$


$$I_B^{\text{Middle}} = \frac{300 \text{ MVA}}{\sqrt{3} \cdot 138 \text{ kV}} = 1250 \text{ Amps} \quad (\text{same current!})$$

$$I_{\text{Middle}}^{\text{Actual}} = 0.22 \angle -30.8^\circ \times 1250 \text{ Amps} = 275 \angle -30.8^\circ \text{ A}$$

3 ϕ Per-Unit Example 2



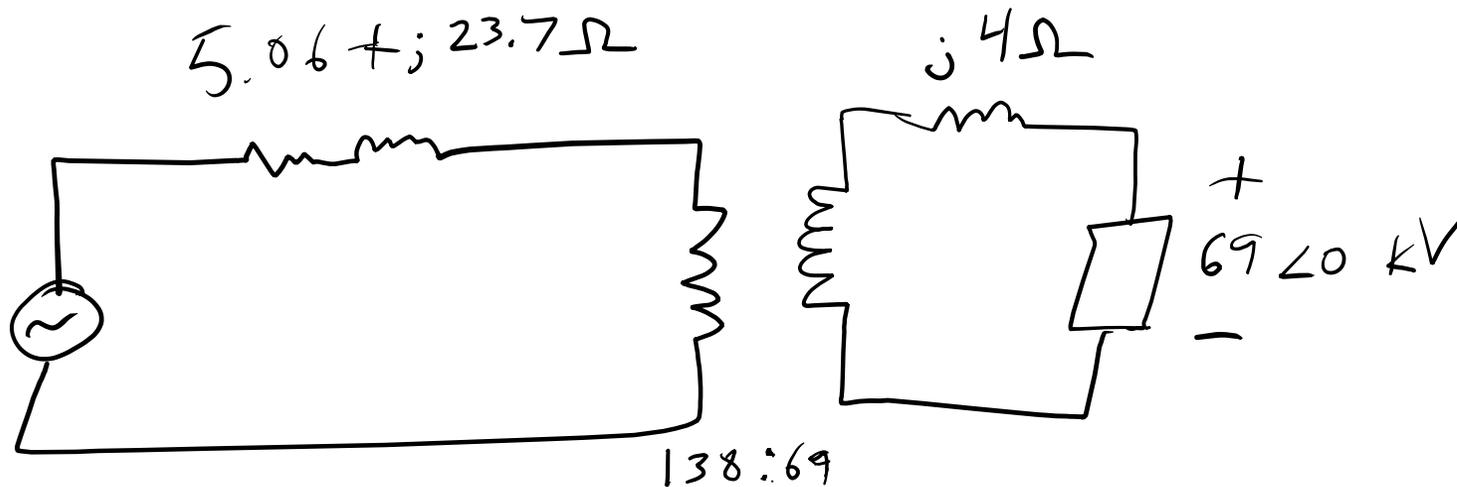- Assume a 3 ϕ load of $100+j50$ MVA with V_{LL} of 69 kV is connected to a source through the below network:



What is the supply current and complex power?

Answer: $I=467$ amps, $S = 103.3 + j76.0$ MVA