

ECEN 460, Spring 2026

Power System Operation and Control

Class 13: Newton-Raphson Solution Method for the Power Flow Problem

Prof. Adam Birchfield

Dept. of Electrical and Computer Engineering

Texas A&M University

abirchfield@tamu.edu



TEXAS A&M
UNIVERSITY

Announcements



- Homework #5: book problems 6.30 and 6.31, due Thursday, Feb. 26, 2026
- Homework #6: book problems 6.9, 6.12, 6.18, 6.25, 6.38, due Thursday, Mar 5, 2026

Recall, Transmission Line and Transformer Models



- Transmission lines use the "pi" model

These devices
reduce down
to impedances

- Transformer non-ideal model is simplified with the per-unit system (and neglecting shunt elements)



Recall, Building the Y-Bus Matrix



- Here are the steps for building the Y-bus matrix
 - Start with an NxN matrix of all zeros (N is the number of buses)
 - For any shunt elements (connected to ground, such as most capacitors)
 - Add \bar{Y} to the corresponding diagonal elements of the Y-bus
 - For branches between two buses,
 - Add \bar{Y} to both diagonal elements of the Y-bus
 - Subtract \bar{Y} from both off-diagonal elements of the Y-bus
- We add one network element at a time to the Y-bus matrix!

Remember,
 $\bar{Y} = 1/\bar{Z}$

$$\longrightarrow \begin{bmatrix} \bar{Y}_A + \bar{Y}_B & -\bar{Y}_A & -\bar{Y}_B & 0 \\ -\bar{Y}_A & \bar{Y}_A + \bar{Y}_C + \bar{Y}_D & -\bar{Y}_C & -\bar{Y}_D \\ -\bar{Y}_B & \bar{Y}_C & \bar{Y}_B + \bar{Y}_C & 0 \\ 0 & -\bar{Y}_D & 0 & \bar{Y}_D \end{bmatrix}$$

The Power Flow Problem



- What we know:
 - Generator real power
 - Generator voltage magnitude
 - Load real and reactive power
- What we don't know:
 - Bus voltage angles
 - Non-generator bus voltage magnitude
 - Generator reactive power
 - Current injections of generators or loads
- Note that the problem is formulated with *power* values, not current, so we cannot use the Y-bus equations directly
- Power flow problem is ***non-linear***

Power Flow Problem Variables



- These two equations must be satisfied for all buses in the system
- Total of $2n$ equations
- Parameters g and b are known from the Y-bus
- Each bus has four variables:
 - Bus voltage magnitude V_i
 - Bus voltage angle θ_i
 - Bus real power injection P_i
 - Bus reactive power injection Q_i
- So in general, we need to pre-specify 2 additional variables at each bus before we can solve

$$P_i = \sum_{k=1}^n |V_i||V_k| (g_{ik} \cos \theta_{ik} + b_{ik} \sin \theta_{ik}) = P_{Gi} - P_{Di}$$

$$Q_i = \sum_{k=1}^n |V_i||V_k| (g_{ik} \sin \theta_{ik} - b_{ik} \cos \theta_{ik}) = Q_{Gi} - Q_{Di}$$

Power Flow Bus Types



Each bus has one of three basic types, and for each one there are two known variables and two unknown variables:

- Load (PQ) bus
 - Assume P/Q are fixed at most buses in the system
 - Known: P and Q , Unknown: V and θ
- Slack bus
 - Only one in the whole system
 - Usually assigned to a large generator bus
 - Known: V and θ , Unknown: P and Q
 - Provides angle reference ($\theta = 0$) and picks up the slack P
- Generator (PV) bus
 - Other generators (5-10% of buses in a large system)
 - Assume generator is controlling power output and voltage
 - Known: V and P , Unknown: θ and Q

Using Newton-Raphson to Solve the Power Flow Problem



- Gauss is no longer in wide use for power flow solutions
- Newton-Raphson is the standard method
- Variables are θ and V for every bus (except slack bus)

$$\mathbf{x} = \begin{bmatrix} \theta_2 \\ \vdots \\ \theta_n \\ |V_2| \\ \vdots \\ |V_n| \end{bmatrix} \quad \mathbf{f}(\mathbf{x}) = \begin{bmatrix} P_2(\mathbf{x}) - P_{G2} + P_{D2} \\ \vdots \\ P_n(\mathbf{x}) - P_{Gn} + P_{Dn} \\ Q_2(\mathbf{x}) - Q_{G2} + Q_{D2} \\ \vdots \\ Q_n(\mathbf{x}) - Q_{Gn} + Q_{Dn} \end{bmatrix}$$

$$P_i = \sum_{k=1}^n |V_i||V_k| (g_{ik} \cos \theta_{ik} + b_{ik} \sin \theta_{ik}) = P_{Gi} - P_{Di}$$

$$Q_i = \sum_{k=1}^n |V_i||V_k| (g_{ik} \sin \theta_{ik} - b_{ik} \cos \theta_{ik}) = Q_{Gi} - Q_{Di}$$

Newton-Raphson Power Flow Procedure



Same procedure we have been using for N-R solutions so far

1. Build the Y-bus matrix
2. Write the list the variables and power balance equations
3. Make the power flow Jacobian
4. Make an initial guess of \mathbf{x}

5. While $\|\mathbf{f}(\mathbf{x}^{(v)})\| > \epsilon$

$$\mathbf{x}^{(v+1)} = \mathbf{x}^{(v)} - \mathbf{J}(\mathbf{x}^{(v)})^{-1}\mathbf{f}(\mathbf{x}^{(v)})$$

$$v = v + 1$$

Power Flow Jacobian Matrix



The most difficult part of the algorithm is determining and inverting the n by n Jacobian matrix, $\mathbf{J}(\mathbf{x})$

$$\mathbf{J}(\mathbf{x}) = \begin{bmatrix} \frac{\partial f_1(\mathbf{x})}{\partial x_1} & \frac{\partial f_1(\mathbf{x})}{\partial x_2} & \dots & \frac{\partial f_1(\mathbf{x})}{\partial x_n} \\ \frac{\partial f_2(\mathbf{x})}{\partial x_1} & \frac{\partial f_2(\mathbf{x})}{\partial x_2} & \dots & \frac{\partial f_2(\mathbf{x})}{\partial x_n} \\ \vdots & \ddots & \ddots & \vdots \\ \frac{\partial f_n(\mathbf{x})}{\partial x_1} & \frac{\partial f_n(\mathbf{x})}{\partial x_2} & \dots & \frac{\partial f_n(\mathbf{x})}{\partial x_n} \end{bmatrix}$$

Power Flow Jacobian Matrix, Cont.



Jacobian elements are calculated by differentiating each function, $f_i(\mathbf{x})$, with respect to each variable. For example, if $f_i(\mathbf{x})$ is the bus i real power equation

$$f_i(x) = \sum_{k=1}^n |V_i||V_k| (g_{ik} \cos \theta_{ik} + b_{ik} \sin \theta_{ik}) - P_{Gi} + P_{Di}$$


$$\frac{\partial f_i(x)}{\partial \theta_i} = \sum_{\substack{k=1 \\ k \neq i}}^n |V_i||V_k| (-g_{ik} \sin \theta_{ik} + b_{ik} \cos \theta_{ik})$$

$$\frac{\partial f_i(x)}{\partial \theta_j} = |V_i||V_j| (g_{ij} \sin \theta_{ij} - b_{ij} \cos \theta_{ij}) \quad (j \neq i)$$

Power Flow Example #1



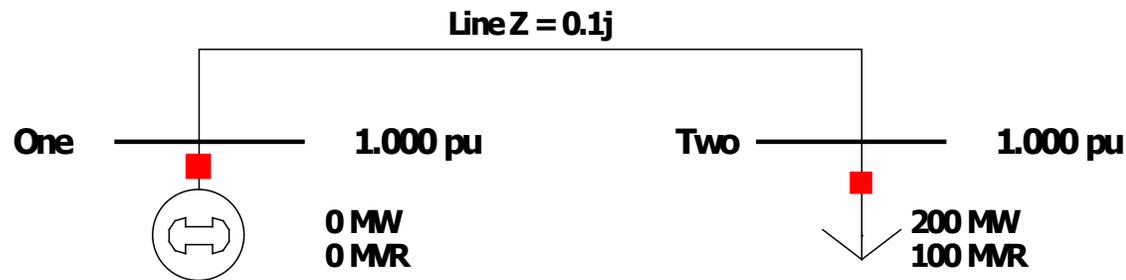- For the two bus power system shown below, use the Newton-Raphson power flow to determine the voltage magnitude and angle at bus two. Assume that bus one is the slack and SBase = 100 MVA.



$$P_i = \sum_{k=1}^n |V_i||V_k| (g_{ik} \cos \theta_{ik} + b_{ik} \sin \theta_{ik}) = P_{Gi} - P_{Di}$$

$$Q_i = \sum_{k=1}^n |V_i||V_k| (g_{ik} \sin \theta_{ik} - b_{ik} \cos \theta_{ik}) = Q_{Gi} - Q_{Di}$$

Power Flow Example #1




Power Flow Example #1



Power Flow Example #1, Solution



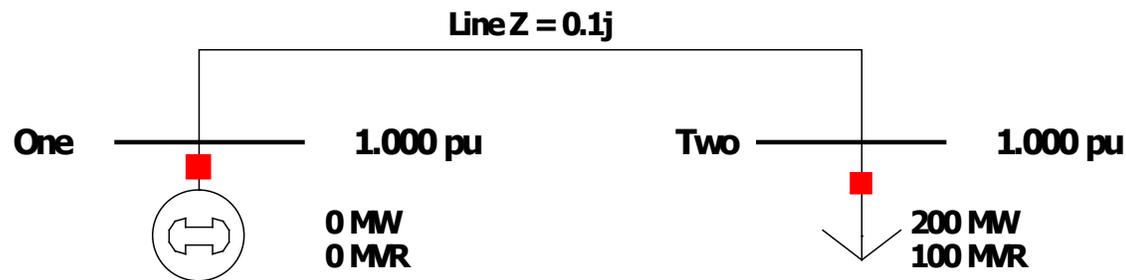- For the two bus power system shown below, use the Newton-Raphson power flow to determine the voltage magnitude and angle at bus two. Assume that bus one is the slack and SBase = 100 MVA.



$$\mathbf{x} = \begin{bmatrix} \theta_2 \\ |V_2| \end{bmatrix} \quad \mathbf{Y}_{bus} = \begin{bmatrix} -j10 & j10 \\ j10 & -j10 \end{bmatrix}$$

General power balance equations

$$P_i = \sum_{k=1}^n |V_i||V_k| (G_{ik} \cos \theta_{ik} + B_{ik} \sin \theta_{ik}) = P_{Gi} - P_{Di}$$

$$Q_i = \sum_{k=1}^n |V_i||V_k| (G_{ik} \sin \theta_{ik} - B_{ik} \cos \theta_{ik}) = Q_{Gi} - Q_{Di}$$

Bus two power balance equations

$$|V_2||V_1|(10 \sin \theta_2) + 2.0 = 0$$

$$|V_2||V_1|(-10 \cos \theta_2) + |V_2|^2(10) + 1.0 = 0$$

Now calculate the power flow Jacobian

$$J(\mathbf{x}) = \begin{bmatrix} \frac{\partial P_2(\mathbf{x})}{\partial \theta_2} & \frac{\partial P_2(\mathbf{x})}{\partial |V|_2} \\ \frac{\partial Q_2(\mathbf{x})}{\partial \theta_2} & \frac{\partial Q_2(\mathbf{x})}{\partial |V|_2} \end{bmatrix}$$

$$= \begin{bmatrix} 10|V_2| \cos \theta_2 & 10 \sin \theta_2 \\ 10|V_2| \sin \theta_2 & -10 \cos \theta_2 + 20|V_2| \end{bmatrix}$$

Power Flow Example #1, Solution Cont.



- Set $v = 0$, guess $\mathbf{x}^{(0)} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$

Calculate

$$f(\mathbf{x}^{(0)}) = \begin{bmatrix} |V_2|(10 \sin \theta_2) + 2.0 \\ |V_2|(-10 \cos \theta_2) + |V_2|^2(10) + 1.0 \end{bmatrix} = \begin{bmatrix} 2.0 \\ 1.0 \end{bmatrix}$$

$$\mathbf{J}(\mathbf{x}^{(0)}) = \begin{bmatrix} 10|V_2| \cos \theta_2 & 10 \sin \theta_2 \\ 10|V_2| \sin \theta_2 & -10 \cos \theta_2 + 20|V_2| \end{bmatrix} = \begin{bmatrix} 10 & 0 \\ 0 & 10 \end{bmatrix}$$

$$\text{Solve } \mathbf{x}^{(1)} = \begin{bmatrix} 0 \\ 1 \end{bmatrix} - \begin{bmatrix} 10 & 0 \\ 0 & 10 \end{bmatrix}^{-1} \begin{bmatrix} 2.0 \\ 1.0 \end{bmatrix} = \begin{bmatrix} -0.2 \\ 0.9 \end{bmatrix}$$

- $f(\mathbf{x}^{(1)}) = \begin{bmatrix} 0.9(10 \sin(-0.2)) + 2.0 \\ 0.9(-10 \cos(-0.2)) + 0.9^2 \times 10 + 1.0 \end{bmatrix} = \begin{bmatrix} 0.212 \\ 0.279 \end{bmatrix}$

$$\mathbf{J}(\mathbf{x}^{(1)}) = \begin{bmatrix} 8.82 & -1.986 \\ -1.788 & 8.199 \end{bmatrix}$$

$$\mathbf{x}^{(2)} = \begin{bmatrix} -0.2 \\ 0.9 \end{bmatrix} - \begin{bmatrix} 8.82 & -1.986 \\ -1.788 & 8.199 \end{bmatrix}^{-1} \begin{bmatrix} 0.212 \\ 0.279 \end{bmatrix} = \begin{bmatrix} -0.233 \\ 0.8586 \end{bmatrix}$$

$$f(\mathbf{x}^{(2)}) = \begin{bmatrix} 0.0145 \\ 0.0190 \end{bmatrix} \quad \mathbf{x}^{(3)} = \begin{bmatrix} -0.236 \\ 0.8554 \end{bmatrix}$$

$$f(\mathbf{x}^{(3)}) = \begin{bmatrix} 0.0000906 \\ 0.0001175 \end{bmatrix} \quad \text{Done! } V_2 = 0.8554 \angle -13.52^\circ$$